PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE - 411043

Department of Electronics & Telecommunication Engineering

INNOVATIVE LEARNING – CROSS WORD

CLASS: SY (E&TCE) (AY: 2025-26, SEM-II) **COURSE: DIGITAL CIRCUITS DESIGN (DCD)**

DAY AND DATE: _____

NAME OF STUDENT:_____**ROLL NO:**_____**DIV:** _____

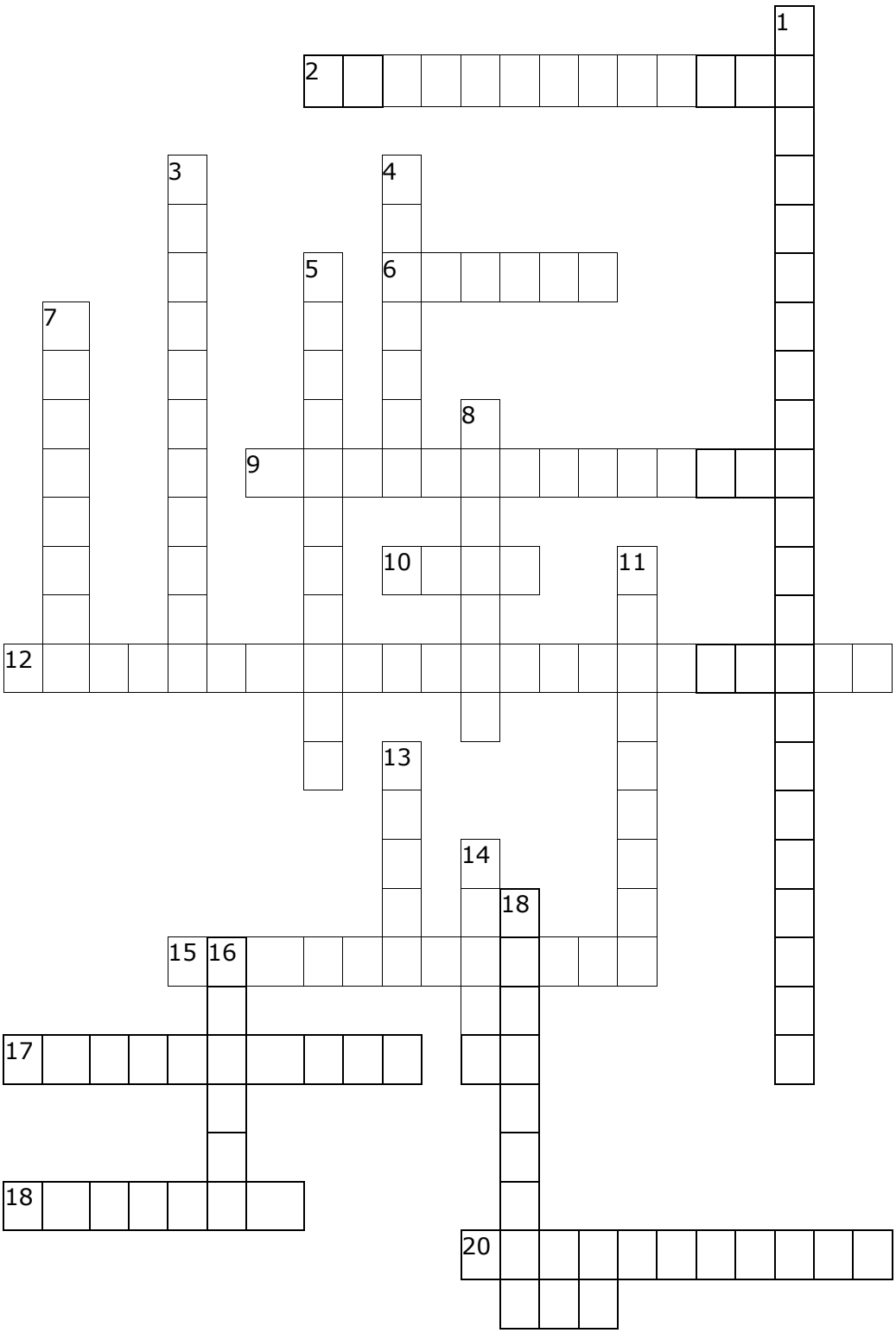

ACROSS:

2. A sequential circuit where only the first flip-flop is clocked by an external clock.

6. Asynchronous counters are often called _____ counters.

9. The circuit can go into the wrong state depending on slight differences in the propagation delays of the gates which is known as _____.

10. A universal gate

12. A fixed architecture logic device with programmable AND gates followed by programmable OR gates.

15. A ripple counter is an _____ counter.

17. Logic circuit used to compare two binary numbers

19. Combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

20. Edge triggered flip flops that uses two latches is called as _____

DOWN:

1. It has programmable and array and fixed or array.

3. A sequence of equally spaced timing pulses may be easily generated by a _____counter

4. Output is high, when any one of the inputs is high

5. Helpful to simplify Boolean expressions with limited inputs

7. A group of flip flops which holds the binary information

8. A sequential circuit which is used to display the number of time any event is repeated or happening.

11. The sequential circuits are designed using the combinational circuits along with a memory device known as _____.

13. The _____ do not have clock input but flip flop has a clock input

14. Asynchronous sequential circuits do not use _____ signals as synchronous circuits do.

16. Enable input is also known as___

18. A shift register that performs all kind of shifts and Parallel Load

DCD Course Teachers:

Mr. Deepak M. Shinde

Dr. Rajendra G. Yelalwar

Ms. Priyanka S. Agnihotri

Dr. Mousami V. Munot